

EE 3340

### Homework Problem #045

In response to an input signal voltage

$$v_s(t) = 24 \cos 2000\pi t \text{ V},$$

the input current in the circuit shown was measured as

$$i(t) = 6 \cos(2000\pi t - 60^\circ) \text{ mA}.$$

Determine the equivalent input impedance  $\mathbf{Z}$  of the circuit.

