

EE 3340  
**Homework Problem #047**

The circuit shown is in the phasor domain. Determine its Thévenin equivalent at terminals  $(a,b)$ .

