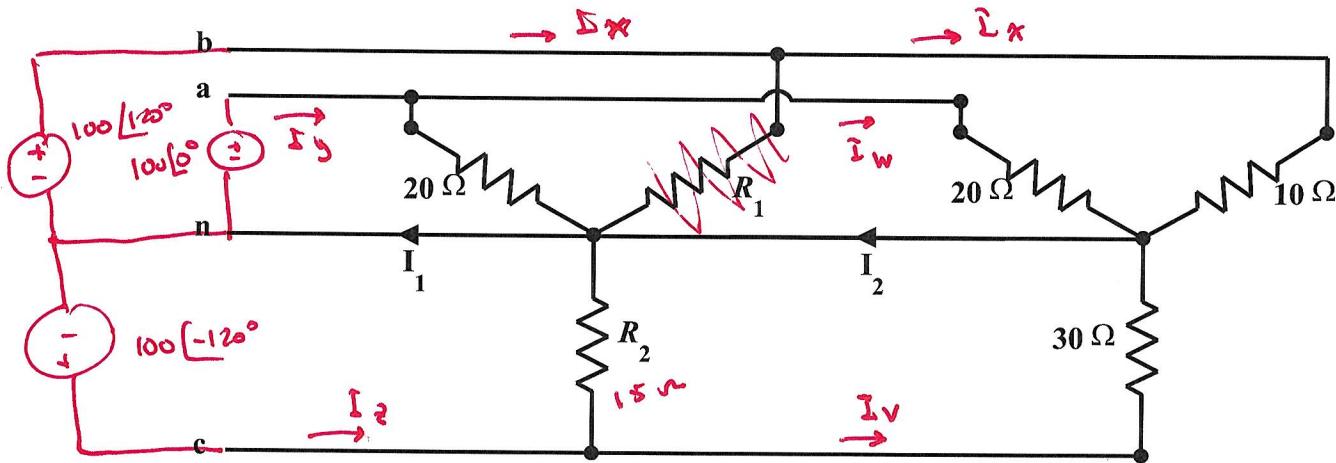


EE 3340  
Homework Problem #048

Given  $v_\phi = 100 \text{ V}$  (i.e.,  $\mathbf{V}_{an} = 100\angle 0^\circ \text{ V}$ ,  $\mathbf{V}_{bn} = 100\angle 120^\circ \text{ V}$  and  $\mathbf{V}_{cn} = 100\angle -120^\circ \text{ V}$ ) for the load shown below, determine  $R_1$  and  $R_2$  so that the sources see a balanced load. Then, find the values of  $\mathbf{I}_1$  and  $\mathbf{I}_2$ .



$$20\Omega \parallel 20\Omega = 10\Omega$$

$\therefore$  Choose  $R_1$  so that  $R_1 \parallel 10\Omega = 10\Omega$   
 $\Rightarrow R_1 = \infty$  (open circuit)

and choose  $R_2$  so that  $R_2 \parallel 30\Omega = 10\Omega$

$$I_x = \frac{100\angle 120^\circ}{10} = 10\angle 120^\circ \text{ A}$$

$$\Rightarrow \frac{30R_2}{30+R_2} = 10$$

$$I_y = \frac{100\angle 0^\circ}{10} = 10\angle 0^\circ \text{ A}$$

$$30R_2 = 300 + 10R_2$$

$$I_z = \frac{100\angle -120^\circ}{10} = 10\angle -120^\circ \text{ A}$$

$$20R_2 = 300$$

$$I_w = \frac{1}{2}I_y = 5\angle 0^\circ \text{ A}$$

$$R_2 = 15\Omega$$

$$I_v = \frac{1}{3}I_z = \frac{10}{3}\angle -120^\circ \text{ A}$$

$$I_2 = I_x + I_w + I_v = 6.009\angle 106.1^\circ \text{ A}$$

$$I_1 = \frac{1}{2}I_y + I_z + \frac{2}{3}I_z = 0 \quad (\text{as expected, since the load is balanced w.r.t. the source})$$