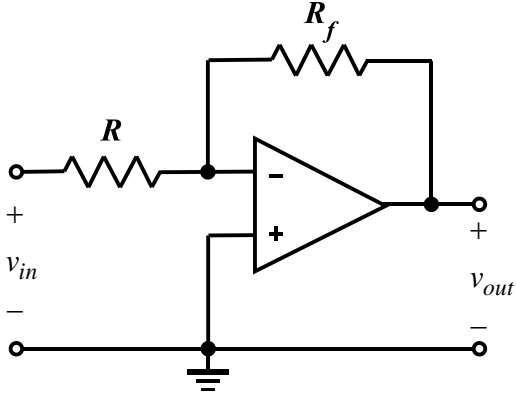
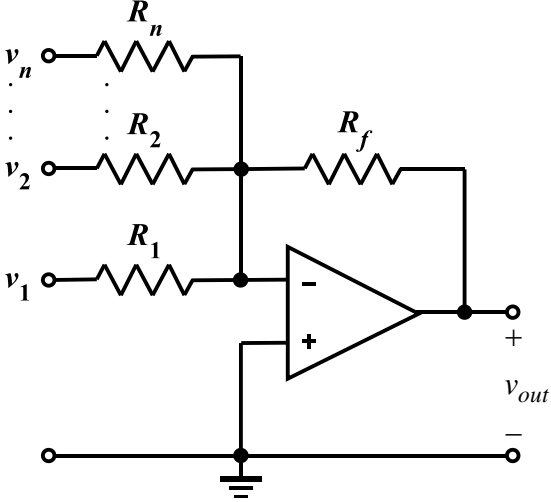
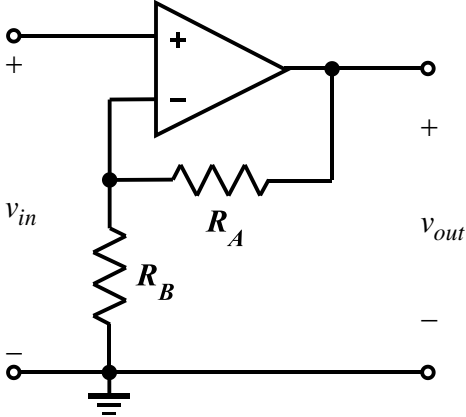
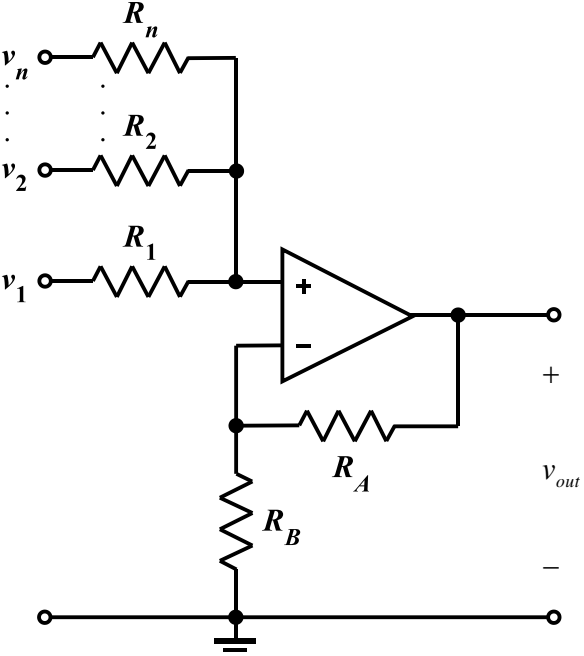
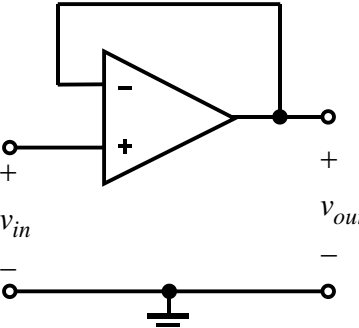
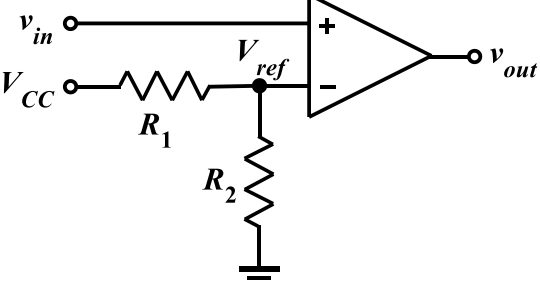
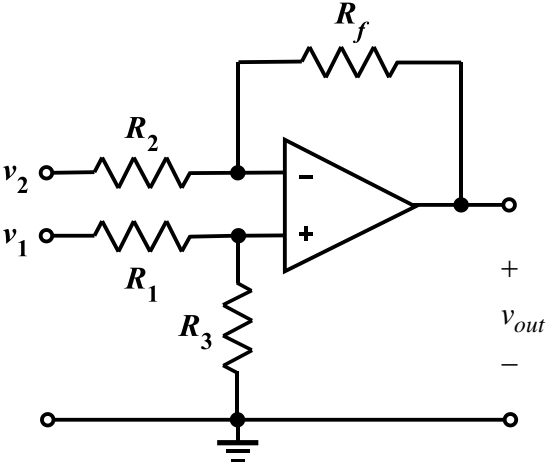
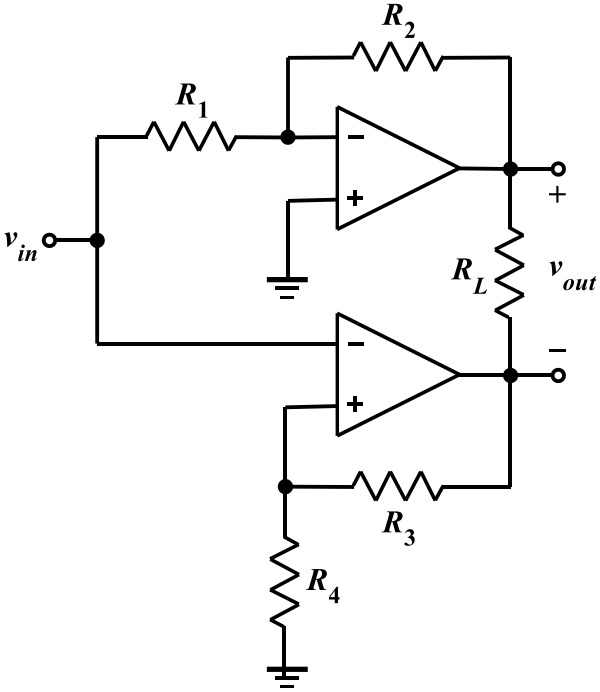
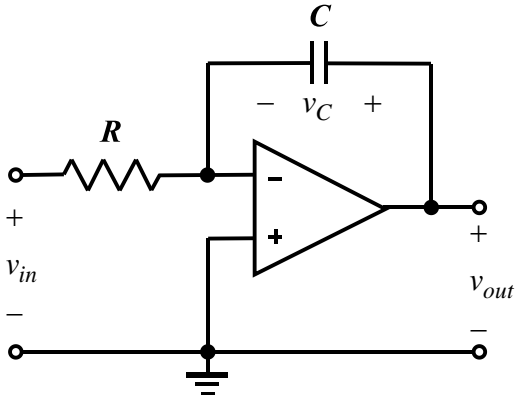
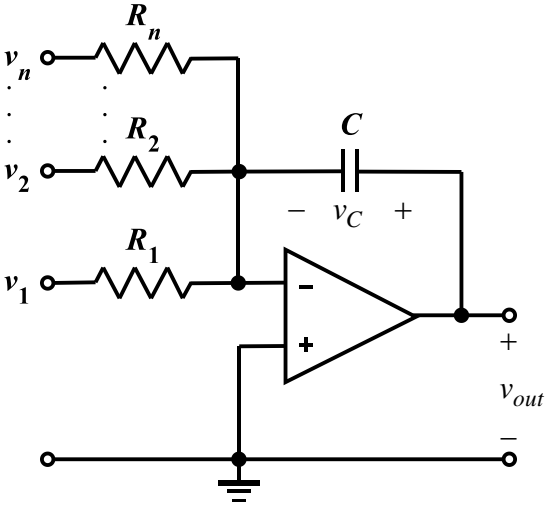
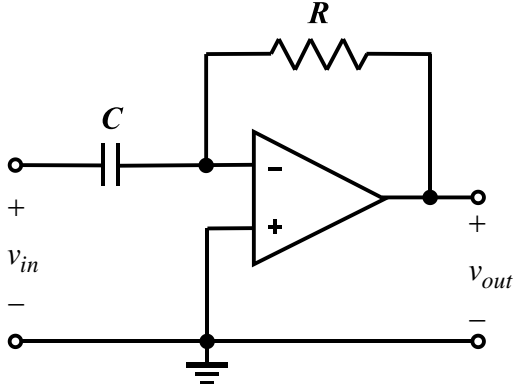
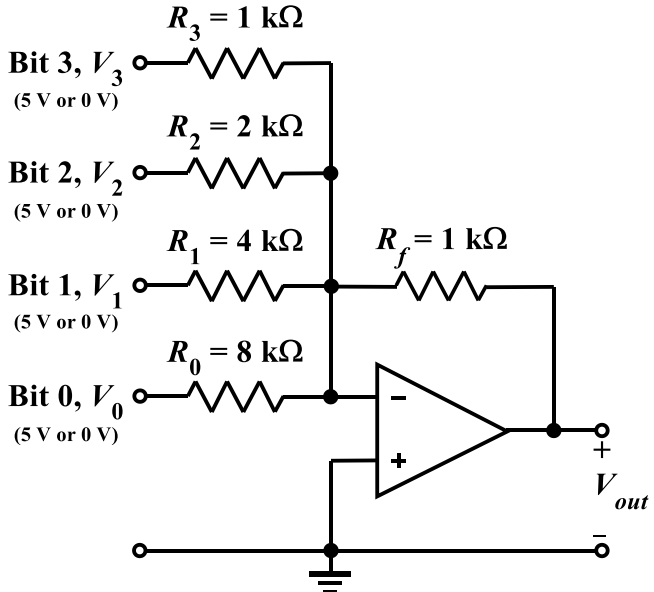


OpAmp Building Blocks

| | Circuit | I/O Relationship |
|--|---|---|
| Inverting Amplifier |  | $v_{out} = -\left(\frac{R_f}{R}\right)v_{in}$ |
| Summing Amplifier, or Summing Inverter, or Adder |  | $v_{out} = -\left(\frac{R_f}{R_1}\right)v_1 - \left(\frac{R_f}{R_2}\right)v_2 \cdots - \left(\frac{R_f}{R_n}\right)v_n$ <p>If $R_f = R_1 = R_2 = \cdots = R_n$, then</p> $v_{out} = -(v_1 + v_2 + \cdots + v_n)$ |
| Non-Inverting Amplifier |  | $v_{out} = \left(1 + \frac{R_A}{R_B}\right)v_{in}$ |

| | | |
|---|---|---|
| <p style="text-align: center;">Non-Inverting Summing Amplifier</p> |  | $v_{out} = \left(1 + \frac{R_A}{R_B}\right) \frac{\left(\frac{1}{R_1} v_1 + \frac{1}{R_2} v_2 + \dots + \frac{1}{R_n} v_n\right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}\right)}$ <p>If $R_1 = R_2 = \dots = R_n$, then</p> $v_{out} = \left(1 + \frac{R_A}{R_B}\right) \left(\frac{v_1 + v_2 + \dots + v_n}{n}\right)$ <p>a) Then, note that if $R_B \rightarrow \infty$,</p> $\lim_{R_B \rightarrow \infty} v_{out} = \frac{1}{n} (v_1 + v_2 + \dots + v_n),$ the average of the inputs. <p>b) Or, if $\frac{R_A}{R_B} = n - 1$, then</p> $v_{out} = v_1 + v_2 + \dots + v_n,$ the sum of the inputs. |
| <p style="text-align: center;">Isolation Amplifier, Buffer, or Voltage Follower</p> |  | $v_{out} = v_{in}$ |
| <p style="text-align: center;">Comparator</p> |  | $V_{ref} = \frac{R_2}{R_1 + R_2} V_{CC}$ $v_{in} > V_{ref} \Rightarrow v_{out} > 0$ $v_{in} < V_{ref} \Rightarrow v_{out} < 0$ |

| | | |
|---|---|--|
| <p style="writing-mode: vertical-rl; transform: rotate(180deg);">Difference Amplifier or Subtractor</p> |  | $v_{out} = \left(\frac{1 + \frac{R_f}{R_2}}{1 + \frac{R_1}{R_3}} \right) v_1 - \left(\frac{R_f}{R_2} \right) v_2$ <p>If $R_f = R_2$ and $R_1 = R_3$, then</p> $v_{out} = v_1 - v_2$ |
| <p style="writing-mode: vertical-rl; transform: rotate(180deg);">Bridge Amplifier</p> |  | $v_{out} = -\frac{R_2}{R_1} v_{in} - \left(1 + \frac{R_3}{R_4} \right) v_{in}$ <p>Neither end of v_{out} is grounded.</p> <p>Also, if $\frac{R_2}{R_1} = 1 + \frac{R_3}{R_4} \triangleq A_v$, then</p> $v_{out} = -2A_v v_{in}$ |
| <p style="writing-mode: vertical-rl; transform: rotate(180deg);">Integrator</p> |  | $v_{out} = -\frac{1}{RC} \int_{-\infty}^t v_{in} dt$ $= v_{out}(0) - \frac{1}{RC} \int_0^t v_{in} dt$ <p>The initial condition is determined by the initial capacitor voltage since $v_{out} = v_C$.</p> |

| | | |
|--|---|---|
| <p style="text-align: center;">Summing Integrator</p> |  | $v_{out} = -\frac{1}{R_1 C} \int_{-\infty}^t v_1 dt - \frac{1}{R_2 C} \int_{-\infty}^t v_2 dt$ $\dots - \frac{1}{R_n C} \int_{-\infty}^t v_n dt$ $= v_{out}(0) - \frac{1}{R_1 C} \int_0^t v_1 dt - \frac{1}{R_2 C} \int_0^t v_2 dt$ $\dots - \frac{1}{R_n C} \int_0^t v_n dt$ <p>The initial condition is determined by the initial capacitor voltage since $v_{out} = v_C$.</p> |
| <p style="text-align: center;">Differentiator</p> |  | $v_{out} = -RC \frac{dv_{in}}{dt}$ |
| <p style="text-align: center;">4-Bit Digital to Analog Converter (Special case of the Summing Amplifier)</p> |  | $V_{out} = -\left(V_3 + \frac{V_2}{2} + \frac{V_1}{4} + \frac{V_0}{8} \right)$ |